


CHAPTER - 19

SOLIDS AND SEMICONDUCTOR DEVICES

SECTION - I

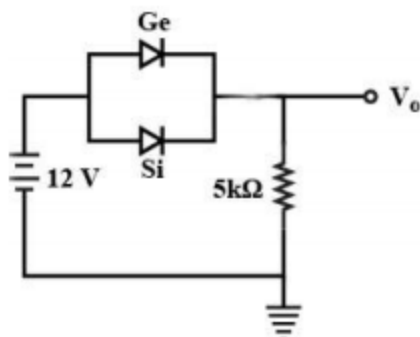1. 4
2. 2
- 3.
4. 4
5. B

Consider the case when Ge and Si diodes are connected as shown in the given figure



Equivalent voltage drop across the combination Ge and Si diode = 0.3 V

$$\Rightarrow \text{Current, } i = \frac{12 - 0.3}{5\text{k}\Omega} = 2.34\text{mA}$$

$$\therefore \text{Output voltage, } V_o = Ri = 5\text{k}\Omega \times 2.34\text{mA} = 11.7\text{V}$$

Now consider the case when diode connection are reversed. In this case voltage drop across the diode's combination = 0.7 V

$$\Rightarrow \text{Current, } i = \frac{12 - 0.7}{5\text{k}\Omega} = 2.26\text{mA}$$

$$\therefore V_o = iR = 2.26\text{mA} \times 5\text{k}\Omega = 11.3\text{V}$$


Hence change in the value of $V_o = 11.7 - 11.3 = 0.4\text{V}$

6. D $V_d = 0.5\text{ V}$, $P = 100\text{ mW} = 100 \times 10^{-3} = 0.1\text{ W}$; $R_d \frac{V_d^2}{P} = \frac{(0.5)^2}{0.1} = 2.5\Omega$; $I_d \frac{V_d}{R_d} = \frac{0.5}{2.5} = 0.2\text{ A}$;

$$\text{Total resistance} = \frac{2.5}{0.2} = 12.5\Omega, R = 12.5 - 2.5 = 10\Omega$$

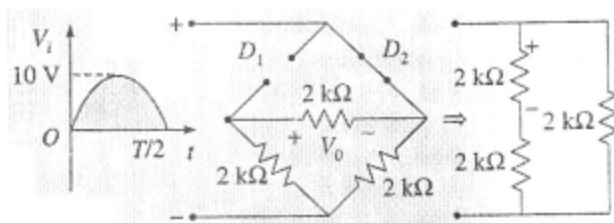7. 4
8. B

For the positive half cycle of input, the resulting network is shown below:



$$\Rightarrow (V_0)_{\max} = \frac{1}{2}(V_i)_{\max} = \frac{1}{2} \times 10 = 5V$$

9. C

10. 2

11. 1

$$12. \quad 3 \quad i = \frac{V}{R} = \frac{20}{2 \times 10^3} = 10 \text{ mA}$$

$$13. \quad 2 \quad R = \frac{\Delta V}{\Delta I} = \frac{2.1 - 2}{(800 - 400) \times 10^{-3}} = \frac{1}{4} = 0.25 \Omega$$

14. 4

15. 4

16. B

A_1	B_1	Y
0	0	1
0	1	1
1	0	1
1	1	0

$$Y = \overline{A_1 \odot B_1} \text{ NAND}$$

$$17. \quad D \quad \overline{(A \cdot A)} = \bar{A}$$

$$\overline{B \cdot B} = \bar{B}$$

$$(\overline{A \cdot B}) = A + B$$

OR Gate

18. D Given circuit represent XOR.

19. C

20. D

21. 5

22. 0.02

23. 199

24. 9

25. 25