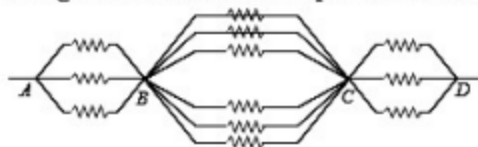


## CHAPTER - 13

# CURRENT ELECTRICITY & CAPACITANCE

1. 3 The given circuit can be simplified as follows




$$\therefore R_{AD} = \frac{5R}{6}$$

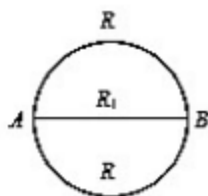2. 3 Resistance across  $AB = \frac{1}{R'} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R_1}$

$$R_1 = 2 \times 10^{-4} \Omega \text{ and } R = \pi \times 1 \times 10^{-4} \Omega$$

$$\text{On solving, } R' = 0.88 \times 10^{-4} \Omega$$



3. 4 Current in the bulb  $= \frac{P}{V} = \frac{4.5}{1.5} = 3A$

$$\text{Current in } 1 \Omega \text{ resistance} = \frac{1.5}{1} = 1.5A$$

$$\text{Hence total current from the cell } i = 3 + 1.5 = 4.5A$$

$$\text{By using } E = V + ir \Rightarrow E = 1.5 + 4.5 \times (2.67) = 13.5V$$


4. 1 Balancing length is independent of the cross sectional area of the wire.

5. 1 In series  $P_{\text{Consumed}} \propto \text{Brightness} \propto \frac{1}{P_{\text{Rated}}}$

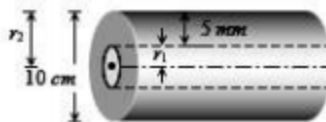6. 1 By using  $R = \rho \cdot \frac{l}{A}$ ; here  $A = \pi(r_2^2 - r_1^2)$

$$\text{Outer radius } r_2 = 5cm$$

$$\text{Inner radius } r_1 = 5 - 0.5 = 4.5cm$$



$$\text{So } R = 1.7 \times 10^{-8} \times \frac{5}{\pi \{(5 \times 10^{-2})^2 - (4.5 \times 10^{-2})^2\}} = 5.6 \times 10^{-5} \Omega$$

7. 3

$$R_{t_1} = R_1(1 + \alpha_1 t) \text{ and } R_{t_2} = R_2(1 + \alpha_2 t)$$

$$\text{Also } R_{eq} = R_{t_1} + R_{t_2} \Rightarrow R_{eq} = R_1 + R_2 + (R_1\alpha_1 + R_2\alpha_2)t$$

$$\Rightarrow R_{eq} = (R_1 + R_2) \left\{ 1 + \left( \frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2} \right) t \right\}$$

$$\text{So } \alpha_{eff} = \frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2}.$$

8. 2

Let the voltage across any one cell is  $V$ , then


$$V = E - ir = E - r_1 \left( \frac{2E}{r_1 + r_2 + R} \right)$$

But  $V = 0$

$$\Rightarrow E - \frac{2Er_1}{r_1 + r_2 + R} = 0$$

$$\Rightarrow r_1 + r_2 + R = 2r_1$$

$$\Rightarrow R = r_1 - r_2$$

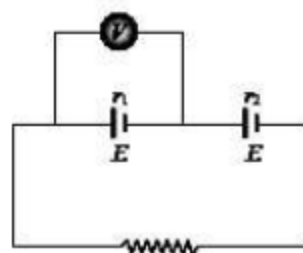

9. 2

In series : Potential difference  $\propto R$

$$\text{When only } S_1 \text{ is closed } V_1 = \frac{3}{4} E = 0.75 E$$

$$\text{When only } S_2 \text{ is closed } V_2 = \frac{6}{7} E = 0.86 E$$

and when both  $S_1$  and  $S_2$  are closed combined resistance of  $6R$  and  $3R$  is  $2R$

$$\therefore V_3 = \left( \frac{2}{3} \right) E = 0.67 E \Rightarrow V_2 > V_1 > V_3$$

10. 2

$$\text{Here, } E = 2V, \quad 1 = \frac{2}{2} = 1A \text{ and } r = 1\Omega$$

$$\text{Therefore, } V = E - ir = 2 - 1 \times 1 = 1V$$

11. 2

12. 2

## SECTION II (NUMERICAL)

13. 10

$$H = \frac{V^2}{R} t$$

Since supply voltage is same and equal amount of heat will produce, therefore

$$\frac{R_1}{t_1} = \frac{R_2}{t_2} \text{ or } \frac{R_1}{R_2} = \frac{t_1}{t_2} \quad \text{.....(i)}$$

$$\text{But } R \propto l \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \quad \text{.....(ii)}$$

$$\text{By (i) and (ii), } \frac{l_1}{l_2} = \frac{t_1}{t_2} \quad \text{.....(iii)}$$

$$\text{Now } l_2 = \frac{2}{3} l_1 \Rightarrow \frac{l_1}{l_2} = \frac{3}{2}$$

$$\therefore \text{By equation (iii), } \frac{3}{2} = \frac{15}{t_2} \Rightarrow t_2 = 10 \text{ minutes}$$

14. 10

$$H = \frac{V^2}{R} t$$

Since supply voltage is same and equal amount of heat will produce, therefore

$$\frac{R_1}{t_1} = \frac{R_2}{t_2} \text{ or } \frac{R_1}{R_2} = \frac{t_1}{t_2} \quad \text{.....(i)}$$

$$\text{But } R \propto l \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \quad \text{.....(ii)}$$



$$\text{By (i) and (ii), } \frac{l_1}{l_2} = \frac{t_1}{t_2} \quad \text{.....(iii)}$$

$$\text{Now } l_2 = \frac{2}{3} l_1 \Rightarrow \frac{l_1}{l_2} = \frac{3}{2}$$

$$\therefore \text{By equation (iii), } \frac{3}{2} = \frac{15}{t_2} \Rightarrow t_2 = 10 \text{ minutes}$$

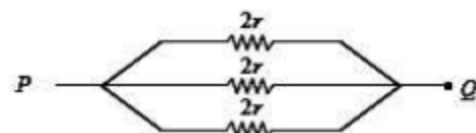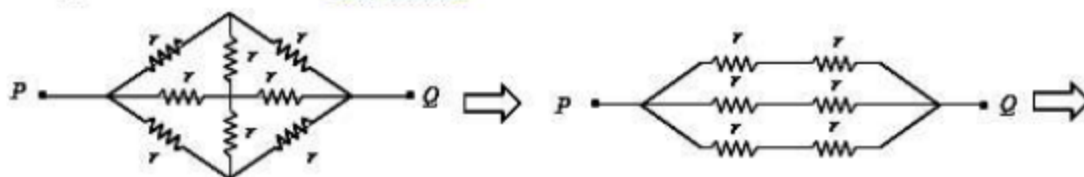15. 1

The given circuit can be simplified as follows



$$R' = \frac{2r}{3} = \frac{2}{3} \times \frac{3}{2} = 1\Omega$$

16. 4 If two resistances are  $R_1$  and  $R_2$  then  $S = R_1 + R_2$  and  $P = \frac{R_1 R_2}{(R_1 + R_2)}$

$$\text{From given condition } S = nP \text{ i.e. } (R_1 + R_2) = n \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\Rightarrow (R_1 + R_2)^2 = n R_1 R_2 \Rightarrow (R_1 - R_2)^2 + 4R_1 R_2 = n R_1 R_2$$


$$\text{So } n = 4 + \frac{(R_1 - R_2)^2}{R_1 R_2}. \text{ Hence minimum value of } n \text{ is } 4.$$

17. 4 Total current through the circuit

$$i = \frac{10}{\frac{1000}{3} + 500} = \frac{3}{250} \text{ A}$$

$$\text{Now voltmeter reading} = i_v \times R_V = \frac{2}{3} \times \frac{3}{250} \times 500 = 4 \text{ V}$$

18. 8

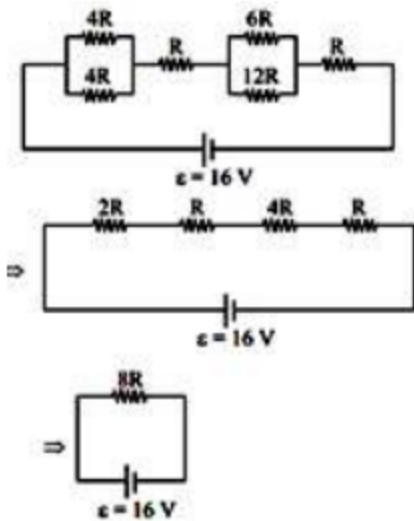


$$P = \frac{16^2}{8R} = 4$$

$$\therefore R = 8 \Omega$$

**JEE ADVANCED LEVEL**  
**SECTION III**

19. B

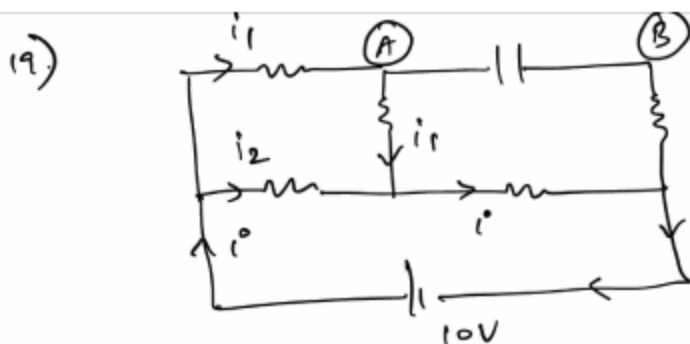

find  $i_1$  and  $i_0$ , Apply KVL between A and B.

20. A


wheat stone application.

21. A

$$\text{Use } P = i^2 R, \quad i^0 = \frac{2}{R+2}$$

$$\therefore P \downarrow$$

22. C

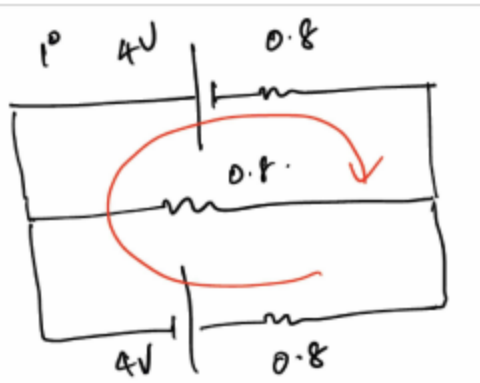

Apply KVL in outside loop,  $i^0 = \frac{8}{1.6} = \frac{10}{2} = 5A$

$$V = 2 - i^0 \cdot 2 \Rightarrow 1 - 0.2 \times 5 = 0V.$$

23. A

$$V = k l, \quad k = \frac{V}{l} = \frac{2R}{(R+2)l}$$

24. D

$$q = q_0 (1 - e^{-t/RC})$$

$$12.6 = 20 (1 - e^{-t/RC})$$

$$0.63 = 1 - e^{-t/RC}$$

$$0.37 = e^{-t/RC} \quad (\text{solve}).$$

Q. CV.

$$20 \mu = 5 \times C$$

$$C = \underline{\underline{4 \mu F}}.$$

**SECTION IV (More than one correct)**

25. A, D

$$P = neAV_d.$$


$$\underline{\underline{AV_d = \text{constant}}}$$

26. A, B

radius.  $r' = r + \left(\frac{2x-r}{1}\right)r$

$x$  - distance from one end.
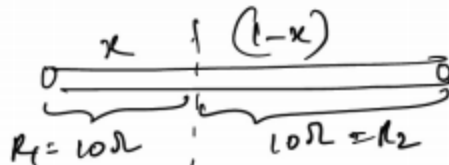
$$\therefore \underline{\underline{r' = r + rx = r(1+x)}}.$$



$$R = \rho \frac{l}{A} = \rho \int \frac{dx}{A} = \rho \int \frac{dx}{\pi r^2 (1+x)^2}$$

$$\begin{aligned}
 R_1 &= \int_0^x \frac{dx}{\pi x^2 (1+x)^2} = \int \frac{dx}{(1+x)^2} \\
 &= (1+x)^{-1} \Big|_0^x \\
 R_1 &\propto \left(1 - \frac{1}{1+x}\right) \\
 R_2 &\propto \left(\frac{1}{(1+x)} - \frac{1}{2}\right) \\
 \frac{2}{1+x} &= \frac{3}{2} \quad 1+x = \frac{4}{3} \\
 x &= \frac{1}{3}
 \end{aligned}$$

27. A,B,C,D

at  $t=0$ , C will offer zero opposition.  $\therefore R_3$  will be shorted


#### SECTION V - (Numerical type)

28. 20

29. 11

Find  $i$  in the circuit, apply KVL rule

30. 1

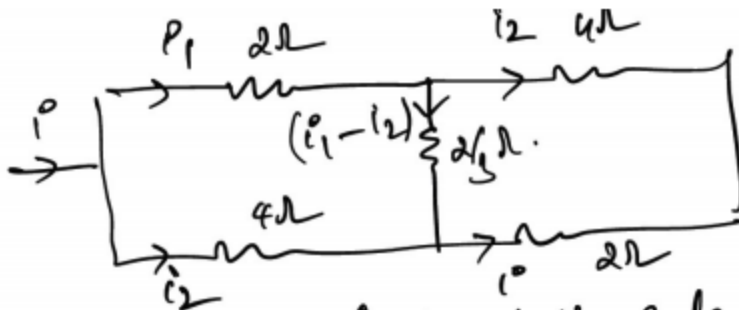

Apply KVL rule and solve.

**SECTION VI - (Matrix match type)**


31. A-q, B-p, C-p

**CAPACITANCE**

**SECTION - I**



1. 2

energy remains same

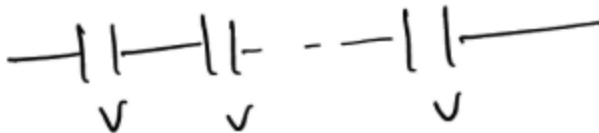

2. 4

← 4V →

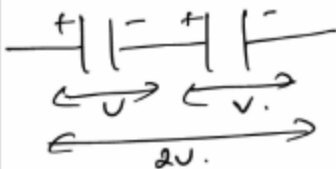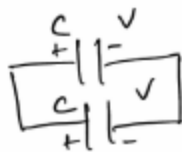



3. 4

$$C = C_1 + C_2$$

$$C = \frac{\epsilon_0 \left( \frac{2A}{3} \right)}{d} + 2 \frac{\epsilon_0 \left( \frac{A}{3} \right)}{d} = \frac{4\epsilon_0 A}{3d}$$

$$c' = \frac{\epsilon_0 A}{d} \therefore C = \frac{4}{3} C^1$$

$$c^1 = \frac{3}{4} c$$

4. 1

$$\frac{C_1}{C_2} = \frac{k_1 \epsilon_0 A / d_1}{k_2 \epsilon_0 A / d_2}$$

5. 1

$$V \propto \frac{Q}{C} \quad V \propto \frac{1}{C}$$

$$\therefore C_1 = C_2$$

$$C_1 = \frac{\epsilon_0 A}{d}, \quad \frac{1}{C_2} = \frac{d}{k \epsilon_0 A} + \frac{t}{\epsilon_0 A}$$

## SECTION II (NUMERICAL)

6. 0

7.  $2\mu\text{F}, 18\mu\text{F}$

## PART II - (JEE ADVANCED LEVEL)

### SECTION - III (One correct answer)

8. D On bringing them in contact,  $V$  becomes same

$$\frac{k(Q_1 - q)}{R_1} = \frac{k(Q_2 + q)}{R_2}$$

$$q = \underline{\hspace{2cm}}$$

$$Q_1' = Q_1 - q$$

$$Q_2' = Q_2 + q$$


$$\Delta U = U_{\text{final}} - U_{\text{initial}}$$

9. A  $\frac{Q_1 + Q_2 + Q_3}{3}$ , using the notion  $E = 0$  inside a conductor.


**SECTION - IV (More than one correct answer)**

10. A, C

$$\begin{array}{c} \frac{Q_1 + Q_2}{2} \left( \frac{Q_1 - Q_2}{2} \right) \\ \left( A \right) \left| \begin{array}{c} \frac{Q_1 + Q_2}{2} \\ - \left( \frac{Q_1 - Q_2}{2} \right) \end{array} \right| \left( B \right) \end{array} \quad \begin{array}{l} V = \frac{Q}{C} \\ V = \frac{(Q_1 - Q_2)/2}{3A/d} \end{array}$$

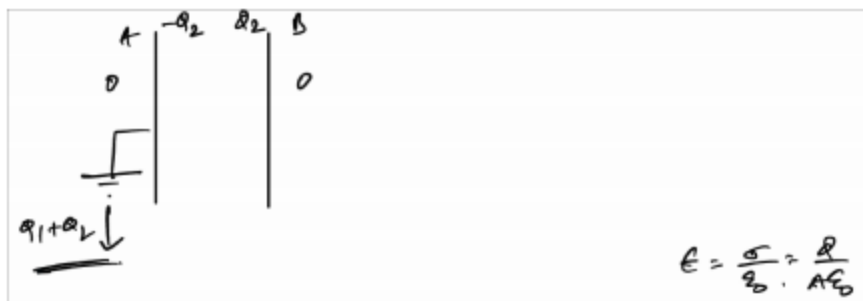


11. A,B,C,D

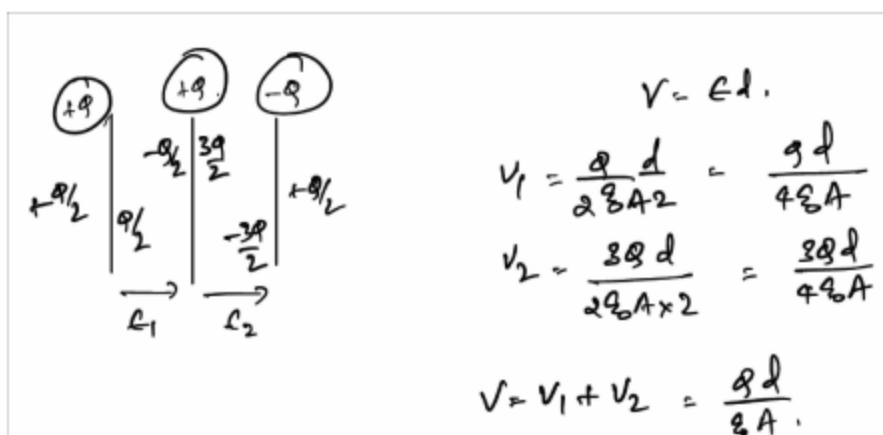

12. B,C,D

find charge on 7μF =  
 same is the charge on 3μF.  
 find voltage across 3μF. Then  
 add voltage across 3μF and 7μF  
 which will be same as voltage across 3.9μF  
 so on...

13. B,C

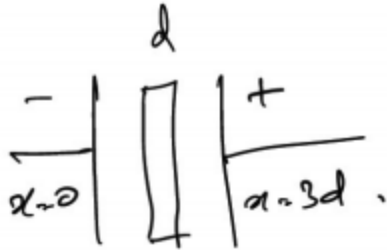

"E direction is same but magnitude changes inside dielectric E decreases.


**SECTION - V (Numerical Type - Upto two decimal place)**

14. 3

$$C_{eff} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_1 = \frac{k_1 \epsilon_0 A}{d_1}, C_2 = \frac{k_2 \epsilon_0 A}{d_2}$$

15. 2

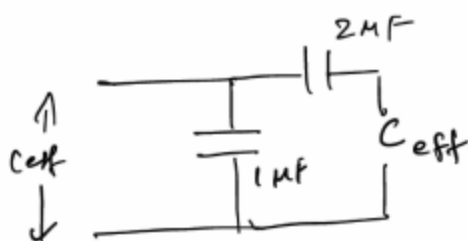

$$\frac{2C_{eff}}{2 + C_{eff}} + 1 = C_{eff} \quad (\text{solve}).$$

16. 5

similar to Q. no. 5.

**SECTION - VI (Matrix Matching)**

17. A-p, B-r,s, C-p, D-r

